



---

---

# COMPUTER ORGANIZATION (ECS 409)

HARDWARE DESCRIPTION LANGUAGE AND VERILOG

Dr. Sukarn Agarwal

EECS  
Indian Institute of Science Education and Research Bhopal

---

---

## Agenda for Today and Next Lecture

---

- Hardware Description Languages
- Implementing Combinational Logic (in Verilog)
- Implementing Sequential Logic (in Verilog)

## Required Readings

---

- [Hardware Description Languages and Verilog](#)
  - H&H Chapter 4 in full

## Grading Policy

### Marks Distribution:

- Assignment: For Practise
- Mid Sem: 40%
- End Sem: 60%


### Assignment Type:

- Implementing Combinational Circuit in Verilog
- Using Structural **Verilog Module Coding**
- Using Behavioral Verilog Module Coding
- Implementing Sequential Circuit in **Verilog**
- Latches, **Counters and Registers**
- State Diagram

# Hardware Description Languages & Verilog

## 2017: Intel Kaby Lake


---

 

[https://en.wikipedia.org/wiki/intel/microarchitectures/kaby\\_lake](https://en.wikipedia.org/wiki/intel/microarchitectures/kaby_lake)

- 64-bit processor
- 4 cores, 8 threads
- 14-19 stage pipeline
- 3.9 GHz clock freq.
- **1.75B transistors**
- In ~47 years, about 1,000,000-fold growth in transistor count and performance!

## 2021: Apple M1

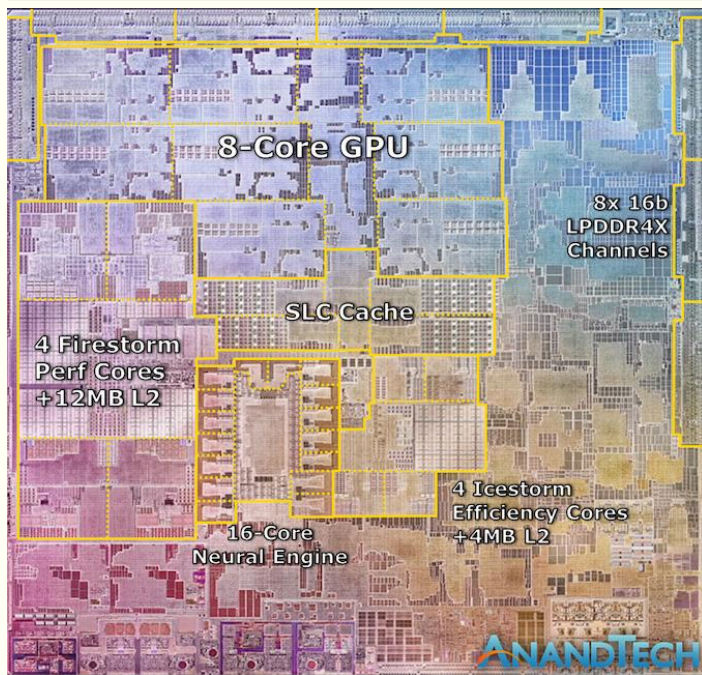


- 4 High-Perf GP Cores
- 4 Efficient GP Cores
- 8-Core GPU
- 16-Core Neural Engine
- Lots of Cache
- Many Caches
- 8x Memory Channels
  
- 16B transistors

Source: <https://www.anandtech.com/show/16252/mac-mini-apple-m1-tested>

## 2022: Apple M1 Ultra

---

 


- 16 High-Perf GP Cores
- 4 Efficient GP Cores
- 64-Core GPU
- 32-Core Neural Engine
- Lots of Cache
- Many Caches
- 32x Memory Channels
- 128 GB DRAM
  
- **114B transistors**

<https://www.theverge.com/2022/3/9/22968611/apple-m1-ultra-gpu-nvidia-rtx-3090-comparison>



## 2019: Cerebras Wafer Scale Engine

---

 

**Cerebras WSE**  
**1.2 Trillion transistors**  
**46,225 mm<sup>2</sup>**

- The largest ML accelerator chip (2019)
- 400,000 cores




**Largest GPU**  
**21.1 Billion transistors**  
**815 mm<sup>2</sup>**

<https://www.anandtech.com/show/14758/hot-chips-31-live-blogs-cerebras-wafer-scale-deep-learning>

<https://www.cerebras.net/cerebras-wafer-scale-engine-why-we-need-big-chips-for-deep-learning/>

## 2021: Cerebras Wafer Scale Engine 2

---

 

**Cerebras WSE-2**  
**2.6 Trillion transistors**  
**46,225 mm<sup>2</sup>**

- The largest ML accelerator chip (2021)
- 850,000 cores



**Largest GPU**  
**54.2 Billion transistors**  
**826 mm<sup>2</sup>**

<https://www.anandtech.com/show/14758/hot-chips-31-live-blogs-cerebras-wafer-scale-deep-learning>  
<https://www.cerebras.net/cerebras-wafer-scale-engine-why-we-need-big-chips-for-deep-learning/>

# Transistor Counts Are Growing

---

Year	Component	Name	Number of MOSFETs (in billions)
2022	Flash memory	Micron's V-NAND chip	5,333 (stacked package of sixteen 232-layer 3D NAND dies)
2020	any processor	Wafer Scale Engine 2	2,600 (wafer-scale design consisting of 84 exposed fields (dies))
2022	microprocessor (commercial)	M1 Ultra	114 (dual-die SoC; entire M1 Ultra is a multi-chip module)
2022	GPU	Nvidia H100	80
2020	DLP	Colossus Mk2 GC200	59.4

In terms of computer systems that consist of numerous integrated circuits, the supercomputer with the highest transistor count as of 2016 is the Chinese-designed Sunway TaihuLight, which has for all CPUs/nodes combined "about 400 trillion transistors in the processing part of the hardware" and "the DRAM includes about 12 quadrillion transistors, and that's about 97 percent of all the transistors."<sup>[9]</sup> To compare, the smallest computer, as of 2018 dwarfed by a grain of rice, has on the order of 100,000 transistors.

**Memory chips have orders of magnitude more transistors than computation chips**

Source: [https://en.wikipedia.org/wiki/Transistor\\_count](https://en.wikipedia.org/wiki/Transistor_count)

## How to Deal with this Complexity?

---

- Hardware Description Languages
- What we need for hardware design:
  - Ability to describe (specify) complex designs
  - ... and to simulate their behavior (functional & timing)
  - ... and to synthesize (automatically design) portions of it
    - have an error-free path to implementation
- Hardware Description Languages enable all of the above
  - Languages designed to describe hardware
  - There are similarly-featured HDLs (e.g., Verilog, VHDL, ...)
    - if you learn one, it is not hard to learn another
    - mapping between languages is typically mechanical, especially for the commonly used subset

# Hardware Description Languages

---

- **Two well-known hardware description languages**


- **Verilog**

- Developed in 1984 by Gateway Design Automation
- Became an IEEE standard (1364) in 1995
- More popular in US

- **VHDL (VHSIC Hardware Description Language)**

- Developed in 1981 by the US Department of Defense
- Became an IEEE standard (1076) in 1987
- More popular in Europe

- We will use Verilog in this course

 

## Why Specialized Languages for Hardware?

- HDLs enable easy description of hardware structures
  - Wires, gates, registers, flip-flops, clock, rising/falling edge, ...
  - Combinational and sequential logic elements
- HDLs enable seamless expression of parallelism inherent in hardware
  - All hardware logic operates concurrently
- Both of the above ease **specification, simulation & synthesis**

# Hardware Design Using HDL

## Key Design Principle: Hierarchical Design

- **Design a hierarchy of modules**


- Predefined “primitive” gates (AND, OR, ...)
- Simple modules are built by instantiating these gates (e.g., components like MUXes)
- Complex modules are built by instantiating simple modules, ...

- **Hierarchy controls complexity**

- Analogous to the use of function/method abstraction in programming

- **Complexity is a BIG deal**

 - In real world, how big is the size of a module (that is described in HDL and then synthesized to gates)?




<https://techreport.com/review/21987/intel-core-i7-3960x-processor>


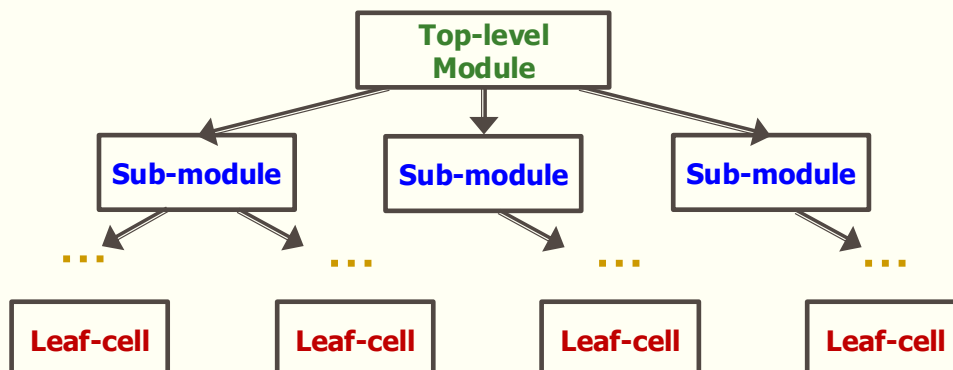
# Top Down Design Methodology

---


- We define the **top-level module** and identify the sub-modules necessary to build the top-level module
- Subdivide the sub-modules until we come to **leaf cells**
  - **Leaf cell**: circuit components that cannot further be divided (e.g., *logic gates, primitive cell library elements*)


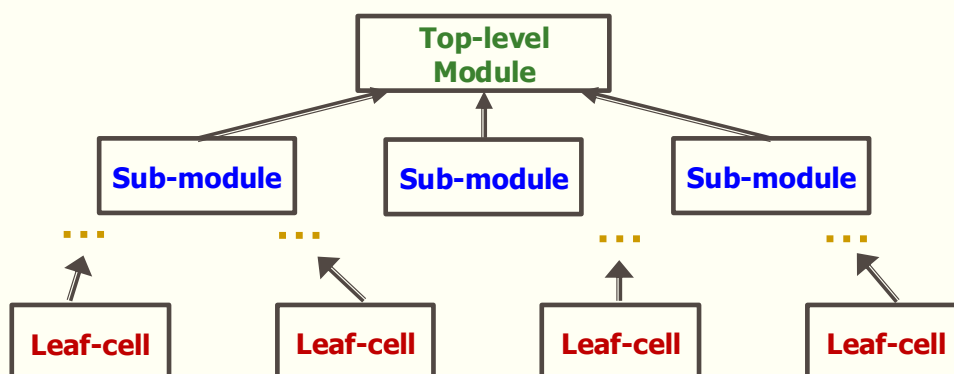
## Bottom Up Design Methodology

---


- We first identify the **building blocks** that are available to us
- **Build bigger modules**, using these building blocks
- These modules are then used for higher-level modules until we build the **top-level module** in the design



 
## Defining a Module in Verilog

---

- A **module** is the main building block in Verilog
- We first need to define:
  - **Name** of the module
  - **Directions** of its **ports** (e.g., **input**, **output**)
  - **Names** of its **ports**
- Then:
  - Describe the **functionality** of the module



# Implementing a Module in Verilog

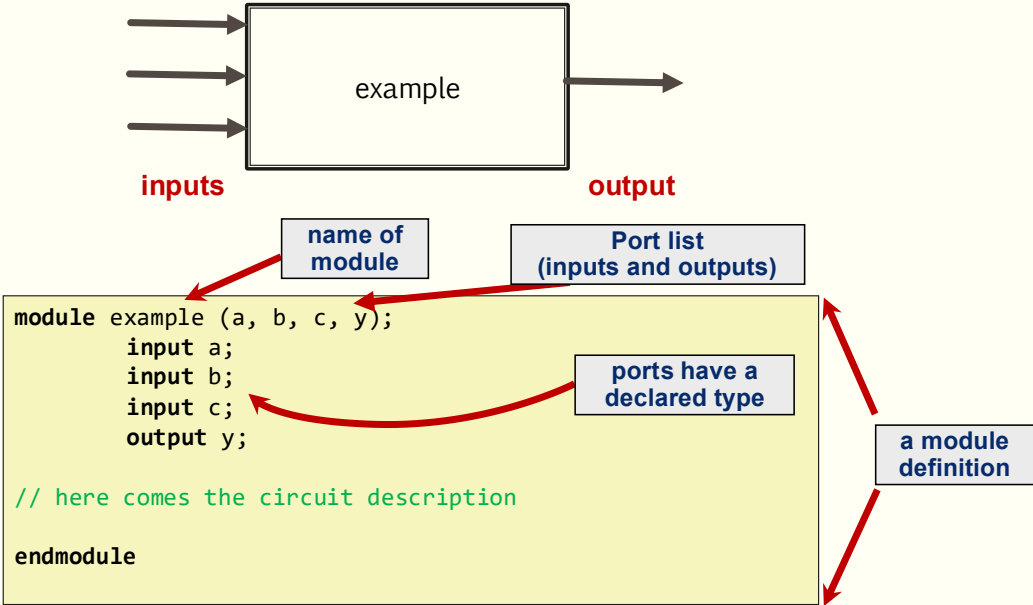

## A Question of Style (and Consistency)

---

- **The following two codes are functionally identical**

```
module test ( a, b, y );  
    input a;  
    input b;  
    output y;  
  
endmodule
```

```
module test ( input a,  
             input b,  
             output y );  
  
endmodule
```

port name and direction declaration  
can be combined

## What If We Have Multi-bit Input/Output?

---

- **You can also define multi-bit Input/Output (Bus)**

- [range\_end : range\_start]
- **Number of bits:** range\_end – range\_start + 1

- **Example:**

```
input  [31:0] a;    // a[31], a[30] .. a[0]
output [15:8] b1;  // b1[15], b1[14] .. b1[8]
output [7:0] b2;  // b2[7], b2[6] .. b2[0]
input          c;  // single signal
```

- **a** represents a 32-bit value, so we prefer to define it as: [31:0] a
- It is preferred over [0:31] a which resembles *array* definition
- It is good practice to **be consistent** with the representation of multi-bit signals, i.e., always [31:0] or always [0:31]

## Manipulating Bits

---

- Bit Slicing
- Concatenation
- Duplication

```
// You can assign partial buses
wire [15:0] longbus;
wire [7:0] shortbus;
assign shortbus = longbus[12:5];

// Concatenating is by {}
assign y = {a[2],a[1],a[0],a[0]};

// Possible to define multiple copies
assign x = {a[0], a[0], a[0], a[0]}
assign y = { 4{a[0]} }
```

## Basic Syntax

---

- Verilog is case sensitive
  - `SomeName` and `somename` are not the same!
- Names cannot start with numbers:
  - `2good` is not a valid name
- Whitespaces are ignored

```
// Single line comments start with a //  
  
/* Multiline comments  
   are defined like this */
```



## Two Main Style of HDL Implementation

---

### ▪ **Structural (Gate-Level)**

- The module body contains **gate-level description** of the circuit
- Describe how modules are interconnected
- Each module contains other modules (instances)
- ... and interconnections between those modules
- Describes a hierarchy of modules defined as gates


### ▪ **Behavioral**

- The module body contains **functional description** of the circuit
- Contains logical and mathematical **operators**
- **Level of abstraction is higher than gate-level**
  - Many possible gate-level realizations of a behavioral description

### ▪ **Many practical designs use a combination of both**

# Structural (Gate-Level) HDL

# Structural HDL: Instantiating a Module

 


**Schematic of module "top" that is built from two instances of module "small"**

# Structural HDL Example
 
## ■ Module Definitions in Verilog

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```
 
# Structural HDL Example

- Defining wires (module interconnections)

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```
 
# Structural HDL Example

- The first instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // instantiate small once  
  small i_first ( .A(A),  
                 .B(SEL),  
                 .Y(n1) );  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```
 
# Structural HDL Example

- The second instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // instantiate small once  
  small i_first ( .A(A),  
                 .B(SEL),  
                 .Y(n1) );  
  
  // instantiate small second time  
  small i_second ( .A(n1),  
                  .B(C),  
                  .Y(Y) );  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

# Structural HDL Example
 
## ■ Short form of module instantiation

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative short form  
  small i_first ( A, SEL, n1 );  
  
  /* In the short form above,  
     pin order very important */  
  
  // safer choice; any pin order  
  small i_second ( .B(C),  
                  .Y(Y),  
                  .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

**Short form is not good practice  
as it reduces code maintainability**



## Structural HDL Example (II)

---

- Verilog supports basic logic gates as predefined *primitives*
  - These primitives are *instantiated* like modules except that they are predefined in Verilog and *do not need a module definition*

```
module mux2(input d0, d1,
            input s,
            output y);
    wire ns, y1, y2;

    not g1 (ns, s);
    and g2 (y1, d0, ns);
    and g3 (y2, d1, s);
    or g4 (y, y1, y2);
endmodule
```

